

# **BASIC ELECTRONICS ENGINEERING**



**(RBL1B002)**

***MODULE-1***

# Clipper Circuits

- The circuit can remove or clip a certain portion of the input signal above / below a specified level is called as Clipper Circuits.
- They are mostly used in digital computers, radars and television.
- They are of 4 types.
  - Positive clipper
  - Negative Clipper
  - Biased Clipper
  - Combination Clipper.



## Positive clippers:

  


## Analysis

For the analysis of the clipper circuits, each half cycles of the input signal must be considered individually.



FOR +Ve HALF CYCLE

  

 - For the +Ve Half cycle of input signal, the general Diodes are reverse biased and hence no current flow
- Therefore,  $I_d = 0\text{v}$  and  $V_R = I_d \times R = 0\text{v}$ , i.e. no output waveform for +Ve half cycle



## FOR -Ve HALF CYCLE

  

- For the -Ve Half cycle of input signal, the diode is forward biased.


- By applying KVL in the loop, we get

$$V_i(t) - V_o - V_D = 0$$

$$\Rightarrow V_o = V_i(t) - V_D$$


If the diode is assumed, Si; Then the output voltage wave form will be

$$V_o = V_i(t) - 0.7v$$

 

If the diode is assumed, Ge; Then the output voltage wave form will be


$$V_o = V_i(t) - 0.3v$$

 





If the diode is assumed, Ideal; Then the output voltage wave form will be


$$V_o = V_i(t) - 0 \text{ v} = V_i(t)$$

 

## Positive clippers:

  

## FOR +Ve HALF CYCLE

 


For the +Ve Half cycle of input signal, the general Diodes are Forward biased and hence current will flow.


Since the Diode is Forward Biased, The Depletion voltage will drop across the Diode e.g. for Si diode (0.7v), for Ge Diode (0.3v), for Ideal diode (0v).

From the circuit, again the output voltage ( $V_o(t)$ ) is same as the diode voltage.

 If the diode is assumed, Si; Then the output voltage wave form will be



 
If the diode is assumed, Ge; Then the output voltage wave form will be



If the diode is assumed, Ideal; Then the output voltage wave form will be




## FOR $-V_e$ HALF CYCLE

 



For the  $-V_e$  Half cycle of input signal, the diode is reverse biased.

Therefore,  $I_d = 0\text{v}$  and  $V_R = I_d \times R = 0\text{v}$

 The net outputs for the input signal  $V_i(t)$  [for different Diodes] are





## Negative clippers:

  

# Analysis

## FOR +V<sub>e</sub> HALF CYCLE

  

## KVL

$$V_i(t) - V_D - V_R = 0$$


$$\Rightarrow V_R = V_i(t) - V_D$$

$$\text{Since, } V_o(t) = V_R$$


$$\text{Therefore, } V_o(t) = V_i(t) - V_D$$



 
If the diode is assumed, Si; Then the output voltage wave form will be



 
If the diode is assumed, Ge; Then the output voltage wave form will be



 If the diode is assumed, ideal; then the output voltage wave form will be





## FOR $-V_e$ HALF CYCLE

 

- In  $-V_e$  half cycle the Diode is reverse Biased and hence no current flow in the path.
- Therefore,  $I_d = 0\text{mA}$  And  $V_R = V_o(t) = 0\text{V}$

## Negative clippers:

  


# Analysis

## FOR +Ve HALF CYCLE


For the +Ve Half cycle of input signal, the general Diodes are reverse biased and hence no current flow.

Therefore,  $I_d = 0$  and  $V_R = I_d \times R = 0$

 $V_o(t) = V_D$  = Maximum voltage drop due to open ckt



## FOR $-V_e$ HALF CYCLE

 



For the  $-V_e$  Half cycle of input signal, the diodes is Forward biased and hence current will flow.

Since the Diode is Forward Biased, The Depletion voltage will drop across the Diode e.g. for Si diode (0.7v), for Ge Diode (0.3v) ,for Ideal diode (0v).


Here the output voltage ( $V_o(t)$ ) is same as the diode voltage
  
## 1. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.



## FOR +V<sub>e</sub> HALF CYCLE

 

As we know that the input signal is higher than the biased voltage.  
Therefore,

For the +V<sub>e</sub> half cycle, the diode is reverse biased and hence no current flow in the path of resistor.



$$I_d = 0\text{v}$$

$$V_R = I_d \times R = 0 \times R = 0\text{v}$$

Since,  $V_o(t) = V_R + 2V$  (because of parallel open loop voltage)

$$\text{Therefore, } V_o(t) = V_R + V = 0\text{v} + 2V = 2\text{ V}$$

## FOR $-V_e$ HALF CYCLE

  

In  $-V_e$  Half cycle the Diode is Forward Biased and hence, there will be a current flow in the path.

Therefore, according to KVL, we get

$$V_i(t) + V - V_R - V_D = 0$$
$$\Rightarrow V_R = V_i(t) + V - V_D$$


Now, we have

$$V_o(t) = V_R - V$$


There fore,  $V_o(t) = V_R - V = V_i(t) - V_D + V - V = V_i(t) - V_D$




If the diode is Si;

 

If the diode is Ge;


 


If the diode is Ideal;


 

  
## 2. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.



## FOR +V<sub>e</sub> HALF CYCLE

 
 


Diode is reverse biased

$\Rightarrow I = 0 \Rightarrow IR = 0 \Rightarrow$  No voltage drop across the resistor

$\Rightarrow V_o = -V$

## FOR $-V_e$ HALF CYCLE

  

Diode is forward biased.

By KVL,




$$V_i - V - IR - V_D = 0$$

$$\Rightarrow V_i - V_D - (V + IR) = 0$$

$$\Rightarrow V_i - V_D - V_o = 0$$



$$\Rightarrow V_o = V_i - V_D$$

   If the diodes are assumed, Si, Ge, Ideal; Then the output voltage wave forms are



  
### 3. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.



## FOR +V<sub>e</sub> HALF CYCLE

 

Diode is forward biased.


By KVL,

$$V_i - V_D - IR - V = 0$$



$$\Rightarrow V_i - V_D - (IR + V) = 0$$

$$\Rightarrow V_i - V_D - V_o = 0$$

$$\Rightarrow V_o = V_i - V_D$$

 

## FOR $-V_e$ HALF CYCLE

  

Diode is reverse biased.




$$\Rightarrow I = 0$$

$\Rightarrow IR = 0 \Rightarrow$  No voltage drop across the resistor.

$$\Rightarrow V_o = V$$





   The net output for the given input signal



  
## 4. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.



## FOR +V<sub>e</sub> HALF CYCLE

 


By KVL

$$V_i(t) - V_D - V_R + V = 0$$



$$\Rightarrow V_i(t) - V_D - (V_R - V) = 0$$

$$\Rightarrow V_i(t) - V_D - V_o(t) = 0$$

$$\Rightarrow V_o(t) = V_i(t) - V_D$$

 

## FOR $-V_e$ HALF CYCLE

  


Diode is reverse biased.

$\Rightarrow$  No current in the loop  $\Rightarrow V_R = 0$


$\Rightarrow V_o(t) = -V$

 The net output for the given input signal




 
## 5. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.





## For +ve half cycle

  

Diode is forward biased.

Here  $V_o = V_D = 0.7$  for Si /  $0.3$  for Ge /  $0$  when diode is ideal

## For -ve half cycle

  

Diode is Reverse biased.

Hence  $I = 0 \Rightarrow V_R = 0$ .


So by KVL

$$-V_i(t) + V - V_o(t) = 0$$

$$\Rightarrow V_o(t) = V - V_i(t)$$





 The net output for the given input signal




  
## 6. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.





## For +ve half cycle

  

Diode is forward biased.

$$\text{So } V_o = V_D$$

## For -ve half cycle

  




Diode is reverse biased.

By KVL,

$$2v + V_i + V_o = 0$$

$$\Rightarrow V_o = - (2v + V_i)$$

   
The net output for the given input signal



**PRACTICE**


 
# 1. Biased clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.


  
## 2. Biased clippers:


Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.




 
### 3. Combination clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.



#### 4. Combination clippers:

Draw the output waveform for the given circuit assuming the diode as Si type, Ge type & Ideal.

